

```

module fifo_sync #(
    parameter DATA_WIDTH = 8,          // Width of each data word
    parameter FIFO_DEPTH = 16          // Depth (number of words)
) (
    input wire clk,
    input wire rst,

    input wire wr_en,                  // Write enable
    input wire rd_en,                  // Read enable

    input wire [DATA_WIDTH-1:0] din,   // Data input
    output reg [DATA_WIDTH-1:0] dout,   // Data output

    output wire full,
    output wire empty,
    output wire almost_full,
    output wire almost_empty
);

// Memory array
reg [DATA_WIDTH-1:0] fifo_mem [0:FIFO_DEPTH-1];

// Write and read pointers (need only log2(FIFO_DEPTH) bits)
localparam PTR_WIDTH = $clog2(FIFO_DEPTH);
reg [PTR_WIDTH-1:0] wr_ptr;
reg [PTR_WIDTH-1:0] rd_ptr;

// Counter to track number of elements in FIFO
reg [PTR_WIDTH:0] fifo_count; // Can count up to FIFO_DEPTH

// Write operation
always @(posedge clk) begin
    if (rst) begin
        wr_ptr <= 0;
    end else if (wr_en && !full) begin
        fifo_mem[wr_ptr] <= din;
        wr_ptr <= wr_ptr + 1;
    end
end

// Read operation
always @(posedge clk) begin
    if (rst) begin
        rd_ptr <= 0;
        dout <= 0;
    end else if (rd_en && !empty) begin

```

```

        dout <= fifo_mem[rd_ptr];
        rd_ptr <= rd_ptr + 1;
    end
end

// FIFO count update
always @(posedge clk) begin
    if (rst) begin
        fifo_count <= 0;
    end else begin
        case ({wr_en && !full, rd_en && !empty})
            2'b10: fifo_count <= fifo_count + 1; // Write only
            2'b01: fifo_count <= fifo_count - 1; // Read only
            2'b11: fifo_count <= fifo_count;      // Simultaneous read and write
            default: fifo_count <= fifo_count;    // No operation
        endcase
    end
end

// Status flags
assign full          = (fifo_count == FIFO_DEPTH);
assign empty         = (fifo_count == 0);
assign almost_full   = (fifo_count >= FIFO_DEPTH - 1);
assign almost_empty  = (fifo_count <= 1);

endmodule

```

```

module alu_top (
    input wire clk,
    input wire rst,
    input wire wr_en,
    input wire [7:0] instr_in, // 8-bit instruction input to FIFO
    input wire exec_en,        // One-cycle pulse to execute instruction from FIFO
    output [7:0] result
);

wire [7:0] instr_out;
wire fifo_empty, fifo_full;

// Internal control
wire [2:0] opcode;
wire [4:0] imm;
reg [7:0] acc;

// Instantiate FIFO (Your existing FIFO)
fifo_sync #(
    .DATA_WIDTH(8),
    .FIFO_DEPTH(16)
) fifo_inst (
    .clk(clk),
    .rst(rst),
    .wr_en(wr_en),
    .rd_en(exec_en),
    .din(instr_in),
    .dout(instr_out),
    .full(fifo_full),
    .empty(fifo_empty)
);

// Decode instruction
assign opcode = instr_out[7:5];
assign imm = instr_out[4:0];

// ALU logic
alu_8bit alu_unit (
    .opcode(opcode),
    .acc(acc),
    .imm(imm),
    .result(result)
);

// Accumulator update
always @(posedge clk) begin
    if (rst)

```

```
        acc <= 0;
    else if (exec_en && !fifo_empty)
        acc <= result;
    end
endmodule
```

```

module alu_8bit (
    input wire [2:0] opcode,
    input wire [7:0] acc,
    input wire [4:0] imm,          // 5-bit immediate
    output reg [7:0] result
);
always @(*) begin
    case (opcode)
        3'b000: result = acc + imm;          // ADDI
        3'b001: result = acc - imm;          // SUBI
        3'b010: result = acc & imm;          // ANDI
        3'b011: result = acc | imm;          // ORI
        3'b100: result = acc ^ imm;          // XORI
        3'b101: result = ~acc;               // NOT (imm ignored)
        3'b110: result = acc + 1;            // INC
        3'b111: result = acc - 1;            // DEC
        default: result = 8'h00;
    endcase
end
endmodule

```

```
timescale 1ns / 1ps
```

```
module alu_top_tb;
```

```
    reg clk;
    reg rst;
    reg wr_en;
    reg exec_en;
    reg [7:0] instr_in;
    wire [7:0] result;
```

```
// Instantiate DUT
```

```
alu_top uut (
    .clk(clk),
    .rst(rst),
    .wr_en(wr_en),
    .instr_in(instr_in),
    .exec_en(exec_en),
    .result(result)
);
```

```
// Clock generation
```

```
always #5 clk = ~clk; // 100 MHz
```

```
// Instruction encoding helper
```

```
function [7:0] encode_instr;
    input [2:0] opcode;
    input [4:0] imm;
    begin
        encode_instr = {opcode, imm};
    end
endfunction
```

```
// Apply a single instruction: write to FIFO, then execute
```

```
task apply_instruction;
    input [2:0] opcode;
    input [4:0] imm;
    begin
        @(negedge clk);
        instr_in = encode_instr(opcode, imm);
        wr_en = 1;
        @(negedge clk);
        wr_en = 0;
        repeat(2) @(negedge clk); // wait until written
        exec_en = 1;
        @(negedge clk);
    end
endtask
```

```

        exec_en = 0;
        repeat(2) @(negedge clk); // wait to observe result
    end
endtask

initial begin
    $display("Starting ALU FIFO Test...");
    $dumpfile("alu_top_tb.vcd");
    $dumpvars(0, alu_top_tb);

    clk = 0;
    rst = 1;
    wr_en = 0;
    exec_en = 0;
    instr_in = 8'h00;

    // Reset the system
    repeat(2) @(negedge clk);
    rst = 0;

    // Test sequence
    // ACC starts at 0

    apply_instruction(3'b000, 5'd10); // ADDI 10    → ACC = 0 + 10 = 10
    $display("ADDI: Result = %d", result);

    apply_instruction(3'b001, 5'd3); // SUBI 3      → ACC = 10 - 3 = 7
    $display("SUBI: Result = %d", result);

    apply_instruction(3'b010, 5'd5); // ANDI 5     → ACC = 7 & 5 = 5
    $display("ANDI: Result = %d", result);

    apply_instruction(3'b011, 5'd2); // ORI 2      → ACC = 5 | 2 = 7
    $display("ORI : Result = %d", result);

    apply_instruction(3'b100, 5'd1); // XORI 1     → ACC = 7 ^ 1 = 6
    $display("XORI: Result = %d", result);

    apply_instruction(3'b101, 5'd0); // NOT        → ACC = ~6 = 8'b11111001 =
    $display("NOT : Result = %d", result);

    apply_instruction(3'b110, 5'd0); // INC        → ACC = 249 + 1 = 250
    $display("INC : Result = %d", result);

    apply_instruction(3'b111, 5'd0); // DEC        → ACC = 250 - 1 = 249

```


```
$display("DEC : Result = %d", result);
```


```
$display("ALU FIFO Test completed.");
```

```
$finish;
```

```
end
```


```
endmodule
```

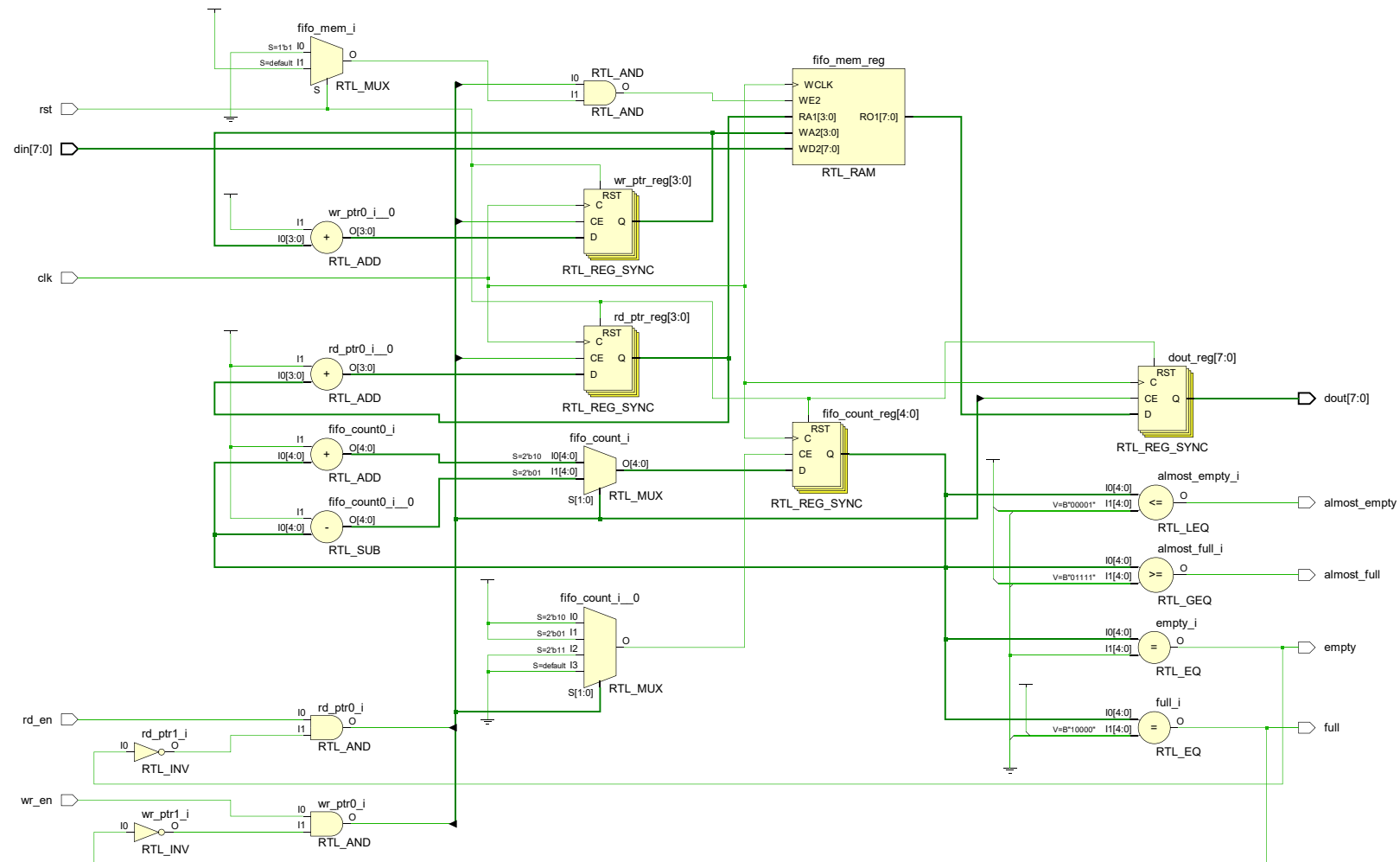

 FIFO_sync.v x alu_top.v x alu_8bit.v x alu_tb.v x **Untitled 18** x

? ? ?

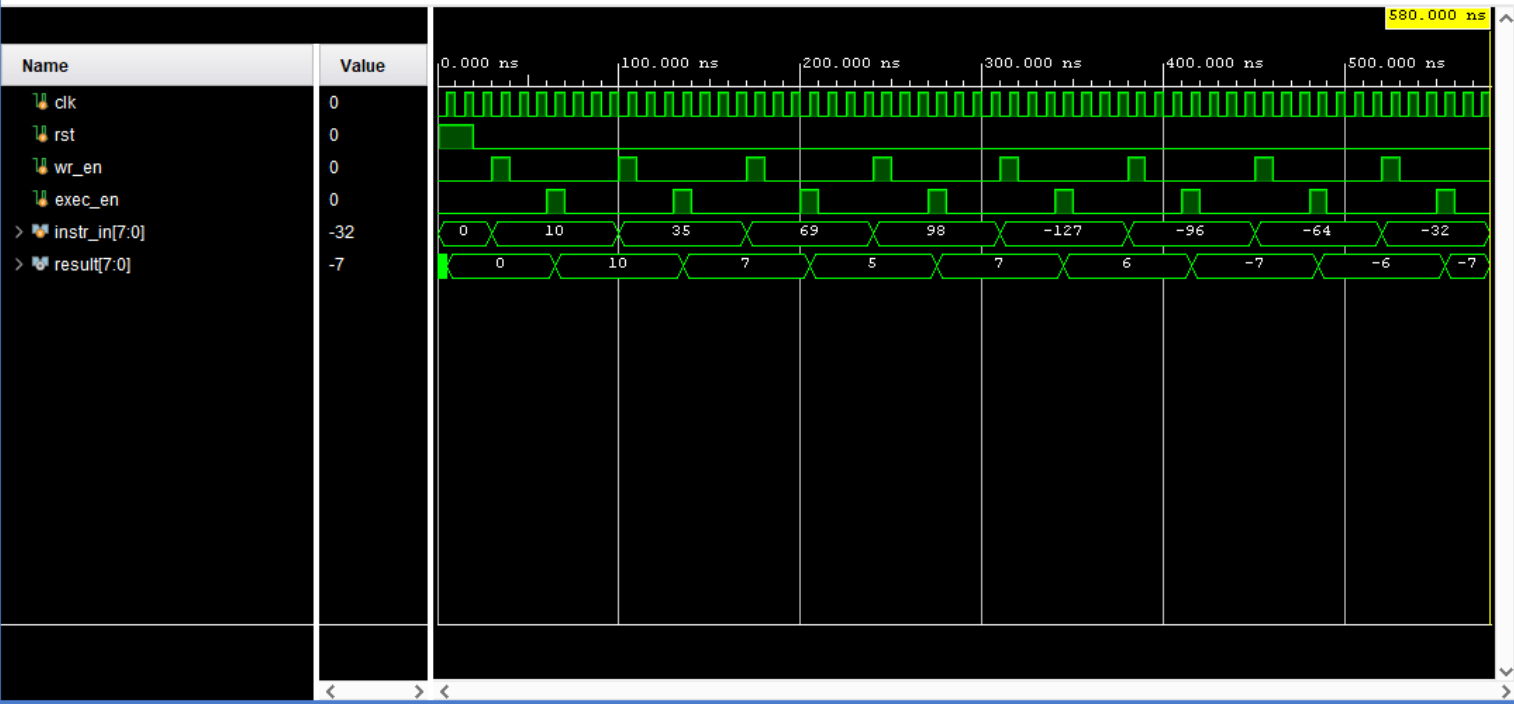

ALU Operation Calculations

ALU Operation Format

Each instruction is 8 bits:

[7:5] Opcode [4:0] Immediate (imm)

Initial State

Accumulator (acc) = 0

Instruction Execution Steps

1. **ADDI 10** (Opcode = 000, imm = 10)

$$acc = 0, \quad imm = 10 \Rightarrow result = acc + imm = 0 + 10 = \boxed{10}$$

2. **SUBI 3** (Opcode = 001, imm = 3)

$$acc = 10, \quad imm = 3 \Rightarrow result = acc - imm = 10 - 3 = \boxed{7}$$

3. **ANDI 5** (Opcode = 010, imm = 5)

$$acc = 7 = 00000111, \quad imm = 5 = 00000101$$

$$result = acc \& imm = 00000101 = \boxed{5}$$

4. **ORI 2** (Opcode = 011, imm = 2)

$$acc = 5 = 00000101, \quad imm = 2 = 00000010$$

$$result = acc | imm = 00000111 = \boxed{7}$$

5. **XORI 1** (Opcode = 100, imm = 1)

$$acc = 7 = 00000111, \quad imm = 1 = 00000001$$

$$result = acc \oplus imm = 00000110 = \boxed{6}$$

6. **NOT** (Opcode = 101, imm ignored)

$$acc = 6 = 00000110$$

$$result = \sim acc = 11111001 = \boxed{249}$$

7. **INC** (Opcode = 110)

$$acc = 249 \Rightarrow result = acc + 1 = \boxed{250}$$

8. **DEC** (Opcode = 111)

$$acc = 250 \Rightarrow result = acc - 1 = \boxed{249}$$

Summary Table of Results

Step	Opcode	Operation	ACC Before	imm	Result	ACC After
1	000	ADDI 10	0	10	10	10
2	001	SUBI 3	10	3	7	7
3	010	ANDI 5	7	5	5	5
4	011	ORI 2	5	2	7	7
5	100	XORI 1	7	1	6	6
6	101	NOT	6	-	249	249
7	110	INC	249	-	250	250
8	111	DEC	250	-	249	249